

Enrollment No: _____

Exam Seat No: _____

C.U.SHAH UNIVERSITY

Summer Examination-2022

Subject Name : Analog and Digital Electronics

Subject Code : 5SC01ADE1

Branch: M.Sc. (Physics)

Semester: 1

Date: 26/04/2022

Time: 11:00 To 02:00

Marks: 70

Instructions:

- (1) Use of a Programmable calculator and any other electronic instrument is prohibited.
- (2) Instructions written in the main answer book are strict to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) in the right places.
- (4) Assume suitable data if needed.

SECTION – I

- Q-1** **Attempt the following questions** **07**
- a. What is an Op-Amp? Give its symbol. **(01)**
 - b. What is a photodiode? Identify its main parts giving its symbol. **(01)**
 - c. What is a phototransistor? Draw its symbol and identify its main parts. **(01)**
 - d. Differentiate UTP and LTP giving their full forms. **(01)**
 - e. What do you mean by the term “Reverse Recovery Time” of a Diode? **(01)**
 - f. Mention any two characteristics of an ideal op-amp. **(02)**
- Q-2** **Attempt all questions** **14**
- (A) What is an LED? Give its Full form. Summarize the Principle, Construction, and Working of LEDs with a suitable symbol, figure and diagram. **(07)**
 - (B) What is an LDR? Give its full form. Write its constructional characteristics. How is an LDR used as an overlight detector? **(07)**
- OR**
- Q-2** Define the terms Clippers and Clampers. Narrate any one of them in detail. **14**
- Q-3** **Attempt all questions** **14**
- (A) Differentiate the Basic Comparator versus Schmitt-Trigger. Write a brief note on Schmitt-Trigger made using an op-amp. **(07)**
 - (B) What is an optocoupler? Elucidate optocoupler with necessary circuit diagram. **(07)**
- OR**
- Q-3** Differentiate Astable, Monostable and Bistable Multivibrators. Discuss in detail any one of them. **14**



SECTION – II

- Q-4** **Attempt the following questions.** **07**
- a. Classify the power amplifiers according to the mode of operation. **(01)**
 - b. Define encoder and decoder. **(01)**
 - c. Define RAM and ROM **(01)**
 - d. Define tuned amplifiers. **(01)**
 - e. Give full forms of DAC and ADC. **(01)**
 - f. Draw the logic diagram of Master-Slave JK Flip-flop. **(02)**
- Q-5** Describe the operation of Half adder and Full adder with a suitable logic diagram, circuit diagram and truth table. Also, explain is the parallel adder? **14**
- OR**
- Q-5** What are the Class-A and Class-B PushPullpower amplifiers? Describe any one of them with a circuit diagram, operation, power distribution and necessary expression. Highlight the advantages and disadvantages. **14**
- Q-6** **Attempt all questions** **14**
- (A) Explain the shift register mode of serial input-serial output with the logic diagram. **(07)**
 - (B) Write a short note on Multiplexers and Demultiplexers. **(07)**
- OR**
- Q-6** Explain basic logic gates with the symbol, truth tables and circuit diagram for each. Also, discuss the universal gates. What are the major applications of the logic gates? **14**

