| Enrollment No: | Exam Seat No: |
|----------------|---------------|
|----------------|---------------|

C.U. SHAH UNIVERSITY

Winter Examination-2022

Subject Name: Fundamentals of Electrical Engineering

Subject Code: 4TE01FEE1 Branch: B.Tech (All)

Semester: 1 Date: 10/01/2023 Time: 11:00 To 02:00 Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
- (2) Instructions written on main answer book are strictly to be obeyed.
- (3) Draw neat diagrams and figures (if necessary) at right places.
- (4) Assume suitable data if needed.

Q-1 Attempt the following questions:

(14)

- a) Kirchhoff's Voltage Law is concerned with
 - (a)IR drops (b) Battery emfs (c) junction voltage (d) both (a) & (b)
- **b)** Hysteresis loss in a magnetic material depends upon
 - (a) area of hysteresis loop (b) frequency of reversal of field
 - (c) Volume of Magnetic Material (d) all of the above
- c) The resistances are having addition in _____ circuit
 - (a) Series

- (b) Parallel
- (c) Both series and parallel
- (d) None of them.
- d) Select the energy Storing elements from the following
 - (a) Resistor

(b) Capacitor

- (c) Both of above
- (d) None of above
- e) The statement for Kirchhoff's Voltage law is represented by
 - (a) V1 + V2 + V3 = 0
- (b) R1 + R2 + R3 = 0
- (c) I1 + I2 + I3 = 0

- (d) None
- f) The frequency term is related with
 - (a) D.C Circuits b) A.C. Circuits c) Both d) Independent Term
- g) Which element can be used as voltage Source
 - (a) Battery

(b) Analog meters

(c) Inductor

- (d) None ot above
- **h)** Define the term Electric flux.
- i) State Ohm's law.
- j) Define the term Electric field intensity.
- **k)** Give definition of voltage.
- 1) Write condition of series resonance.
- m) Define active power in ac system.
- **n)** What is power factor?

| Attem | pt any | four questions from Q-2 to Q-8 | |
|-------|------------|--|-------------|
| Q-2 | | Attempt all questions | (14) |
| | a) | Give the comparison between electrical circuit & magnetic circuit. | (7) |
| | b) | Explain with neat and clean diagram of star to delta transformation. | (7) |
| Q-3 | | Attempt all questions | (14) |
| | a) | Explain briefly about Faraday's laws of electromagnetic induction. | (7) |
| | b) | Derive the equation for the co-efficient of coupling of two magnetically coupled coils A and B. | (7) |
| Q-4 | | Attempt all questions | (14) |
| | a) | State and explain the Kirchhoff's current and voltage laws. | (7) |
| | b) | Derive equation for charging of capacitor in RC circuit. Also define time constant of circuit. | (7) |
| Q-5 | | Attempt all questions | (14) |
| | a) | Define following terms in connection with A.C wave forms: | (7) |
| | | (i) Frequency (ii) Phase difference (iii) Time Period | |
| | | (iv) form factor(v) Peak factor (vi) R.M.S.Value (vii) Average Value | |
| | b) | Prove that current through pure inductor is always lagging by 90° to its voltage and power consumed is zero. | (7) |
| Q-6 | | Attempt all questions | (14) |
| | a) | Three coils each with a resistance of 20Ω and reactance of 20Ω are connected in | (7) |
| | | star across a three phase, 50 Hz, 400V supply. Calculate (a) line current (b)reading | |
| | | on the two wattmeter to measure the power. | |
| | b) | Compare series and parallel resonant circuits. | (7) |
| Q-7 | | Attempt all questions | (14) |
| | a) | Draw and explain the equivalent circuit of single phase transformer. | (7) |
| | b) | Draw and explain the vector diagrams when transformer is on ON-Load condition. | (7) |
| Q-8 | | Attempt all questions | (14) |
| | a) | Explain the method of measuring 3- Φ power by two wattmeters. | (7) |
| | b) | Derive the relation between phase and line values of voltages and currents in | (7) |
| | | balanced star connection. Draw complete phasor diagram of voltages and currents. | |

