

C.U. SHAH UNIVERSITY

Winter Examination-2022

Subject Name: Fundamentals of Electrical Engineering

Subject Code: 4TE01FEE1

Branch: B.Tech (All)

Semester: 1

Date: 10/01/2023

Time: 11:00 To 02:00

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions:

(14)

- a) Kirchoff's Voltage Law is concerned with
(a) IR drops (b) Battery emfs (c) junction voltage (d) both (a) & (b)
- b) Hysteresis loss in a magnetic material depends upon
(a) area of hysteresis loop (b) frequency of reversal of field
(c) Volume of Magnetic Material (d) all of the above
- c) The resistances are having addition in _____ circuit
(a) Series (b) Parallel
(c) Both series and parallel (d) None of them.
- d) Select the energy Storing elements from the following
(a) Resistor (b) Capacitor
(c) Both of above (d) None of above
- e) The statement for Kirchoff's Voltage law is represented by
(a) $V_1 + V_2 + V_3 = 0$ (b) $R_1 + R_2 + R_3 = 0$
(c) $I_1 + I_2 + I_3 = 0$ (d) None
- f) The frequency term is related with
(a) D.C Circuits (b) A.C. Circuits (c) Both (d) Independent Term
- g) Which element can be used as voltage Source
(a) Battery (b) Analog meters
(c) Inductor (d) None of above
- h) Define the term Electric flux.
- i) State Ohm's law.
- j) Define the term Electric field intensity.
- k) Give definition of voltage.
- l) Write condition of series resonance.
- m) Define active power in ac system.
- n) What is power factor?



Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
- a) Give the comparison between electrical circuit & magnetic circuit. (7)
 - b) Explain with neat and clean diagram of star to delta transformation. (7)
- Q-3 Attempt all questions (14)**
- a) Explain briefly about Faraday's laws of electromagnetic induction. (7)
 - b) Derive the equation for the co-efficient of coupling of two magnetically coupled coils A and B. (7)
- Q-4 Attempt all questions (14)**
- a) State and explain the Kirchoff's current and voltage laws. (7)
 - b) Derive equation for charging of capacitor in RC circuit. Also define time constant of circuit. (7)
- Q-5 Attempt all questions (14)**
- a) Define following terms in connection with A.C wave forms: (7)
(i) Frequency (ii) Phase difference (iii) Time Period
(iv) form factor (v) Peak factor (vi) R.M.S. Value (vii) Average Value
 - b) Prove that current through pure inductor is always lagging by 90° to its voltage and power consumed is zero. (7)
- Q-6 Attempt all questions (14)**
- a) Three coils each with a resistance of 20Ω and reactance of 20Ω are connected in star across a three phase, 50 Hz, 400V supply. Calculate (a) line current (b) reading on the two wattmeter to measure the power. (7)
 - b) Compare series and parallel resonant circuits. (7)
- Q-7 Attempt all questions (14)**
- a) Draw and explain the equivalent circuit of single phase transformer. (7)
 - b) Draw and explain the vector diagrams when transformer is on ON-Load condition. (7)
- Q-8 Attempt all questions (14)**
- a) Explain the method of measuring 3- Φ power by two wattmeters. (7)
 - b) Derive the relation between phase and line values of voltages and currents in balanced star connection. Draw complete phasor diagram of voltages and currents. (7)

