

- d) None of the Mentioned
- h)** In ideal Differential Amplifier, if same signal is given to both inputs, then output will be
 - a) Same as input
 - b) Double the input
 - c) Not equal to zero
 - d) Zero
- i)** What is the general information specified in ordering an IC?
 - a) Temperature range
 - b) Device type
 - c) Package type
 - d) All of the mentioned
- j)** Decibel is the unit of _____ gain. (a) Voltage (b) Current (c) Power (d) All
- k)** Which circuit is used for obtaining desired output waveform in operational amplifier?
 - a) Clipper
 - b) Clamper
 - c) Peak amplifier
 - d) Sample and hold
- l)** The clipping level in op-amp is determined by
 - a) AC supply voltage
 - b) Control voltage
 - c) Reference voltage
 - d) Input voltage
- m)** In practical application of current mirror, early voltage is assumed to be
 - a) Infinite
 - b) Zero
 - c) Unity
 - d) None of the mentioned
- n)** Which circuit is used as active load for an amplifier
 - a) Wildar Current source
 - b) Darlington pair
 - c) Current Mirror
 - d) All of the mentioned

Attempt any four questions from Q-2 to Q-8

- Q-2 Attempt all questions (14)**
- (a)** Draw the circuit diagram of differential amplifier with one op-amp and derive the following equations. **(7)**
- a) Closed Loop Voltage Gain b) Input Resistance with Feedback.
- (b)** State the characteristics of an ideal opamp . **(7)**
-
- Q-3 Attempt all questions (14)**
- (a)** State the name of any five parameters those are listed on opamp data sheet. Explain any two. **(7)**
- (b)** Draw the pin diagram of opamp 741 C. Explain the function of each. **(7)**



- Q-4** **Attempt all questions** **(14)**
- (a) Derive the equation of closed loop voltage gain for inverting configuration with feedback. **(7)**
- (b) Briefly discuss about the following: (a) Gain bandwidth product (b) Slew rate (c) Common mode rejection ratio. **(7)**
- Q-5** **Attempt all questions** **(14)**
- (a) State and explain equivalent circuit of an opamp. **(7)**
- (b) Discuss the operation of summing amplifier using opamp. **(7)**
- Q-6** **Attempt all questions** **(14)**
- (a) Draw the circuit diagram of instrumentation amplifier using transducer bridge and explain how it can be used to measure the physical quantity. **(7)**
- (b) Discuss the operation of integrator using opamp. **(7)**
- Q-7** **Attempt all questions** **(14)**
- (a) Discuss the operation of 555 timer in astable mode. **(7)**
- (b) Draw the circuit diagram of op-amp negative clipper circuit and explain its operation with necessary waveforms **(7)**
- Q-8** **Attempt all questions** **(14)**
- (a) Draw the high frequency equivalent circuit of an op-amp and explain that open loop voltage gain of an op-amp is a function of frequency. **(7)**
- (b) Draw the circuit diagram of first order low pass filter and explain its operation. **(7)**

