

Enrollment No: _____

Exam Seat No: _____

C. U. SHAH UNIVERSITY

Winter Examination-2022

Subject Name : Power Electronics II

Subject Code : 4TE07PEL1

Branch: B.Tech (Electrical)

Semester: 7

Date: 21/11/2022

Time: 11:00 To 02:00

Marks: 70

Instructions:

- (1) Use of Programmable calculator & any other electronic instrument is prohibited.
 - (2) Instructions written on main answer book are strictly to be obeyed.
 - (3) Draw neat diagrams and figures (if necessary) at right places.
 - (4) Assume suitable data if needed.
-

Q-1 Attempt the following questions:

(14)

- a) In a Buck converter if, $T_{on} = 1\mu s$, $T_{off} = 2\mu s$, then duty cycle $D =$ _____.
A) $0.5\mu s$ B) $2\mu s$ C) $0.33\mu s$ D) $3\mu s$
- b) The DC-DC converter should be operated at a very low switching frequency.
A) True B) False
- c) A flyback converter is also known by an isolated _____ converter.
A) Boost B) Buck C) Buck-Boost D) None of the above
- d) A forward converter is also known by an isolated _____ converter.
A) Boost B) Buck C) Buck-Boost D) None of the above
- e) Give any two advantages of online UPS over offline UPS.
- f) List any four drawbacks of linear regulated power supply over switch mode power supply.
- g) For a buck converter to reduce the conduction losses in diode _____.
A) high on - resistance switch can be added in parallel
B) low on - resistance switch can be added in parallel
C) A high on - resistance switch can be added in series
- h) The average value of the output voltage in a buck converter is given by
A) $V_0 = V_s$
B) $V_0 = DV_s$
C) $V_0 = V_s/D$
D) $V_0 = V_s / (1 - D)$
- i) Draw block diagram of Switch mode DC supply.
- j) In a steady state operation of DC-DC converter average voltage across the inductor is _____.
A) Finite B) Zero
- k) Give any two advantages of multilevel inverter.
- l) The number of switches used in a half bridge push pull converter is _____.
A) 4 B) 1 C) 2 D) 6
- m) Define resonant converter
- n) Give any two advantages for increasing the number of pulses in rectifier operation.



